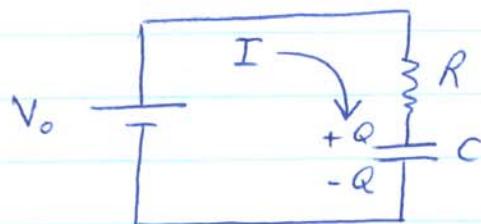


PHYS 2020 Assignment 10

1a)



$V_o = \text{voltage across resistor} + \text{voltage across cap.}$

$$V_o = IR + \frac{Q}{C} \quad \text{where } I = \frac{dQ}{dt}$$

$$\text{b) } V_o = R \frac{dQ}{dt} + \frac{Q}{C}$$

$$R \frac{dQ}{dt} = V_o - \frac{Q}{C}$$


$$\int_0^Q \frac{dQ}{V_o - Q/C} = \int_0^t \frac{dt}{R}$$

$$-C \ln\left(V_o - \frac{Q}{C}\right) \Big|_0^Q = \frac{t}{R}$$

$$\ln\left(\frac{V_o - Q/C}{V_o}\right) = -\frac{t}{RC}$$

$$1 - \frac{Q}{V_o C} = e^{-t/RC}$$
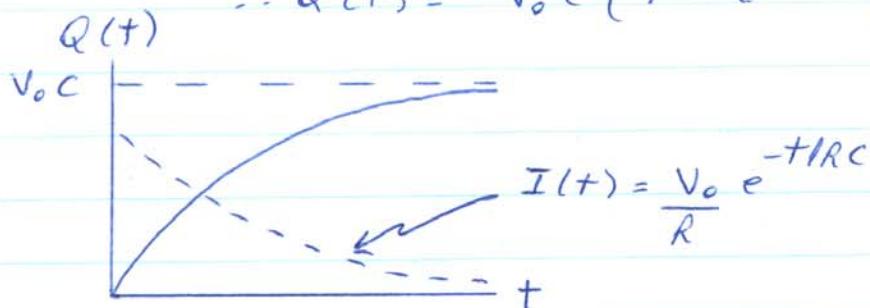
$$\therefore Q(t) = V_o C (1 - e^{-t/RC})$$



$$c) RC = 500 \text{ ohm} \times 2 \times 10^{-6} \text{ farad}$$

$$= 10^{-3} \text{ sec.}$$

$$d) I(t) = \frac{dQ}{dt}$$

$$= \frac{V_0}{R} e^{-t/RC}$$

7.1) Flux through one loop is $\Phi(t) = AB_E \cos \omega t$

where $A = \text{loop area}$ & $B_E = .5 \text{ gauss}$ (earth's field)

$$\text{emf} = -\frac{1}{c} \frac{\partial \Phi}{\partial t}$$


$$= \frac{AB_E \omega \sin \omega t}{c}$$

\therefore max. emf is $\frac{AB_E \omega}{c}$

\therefore max. emf through N loops is

$$\frac{NAB_E \omega}{c} = \frac{4000 \times \pi (12 \text{ cm})^2 \times .5 \text{ gauss} \times 2\pi \times 30 \text{ sec}^{-1}}{3 \times 10^{10} \text{ cm/sec.}}$$
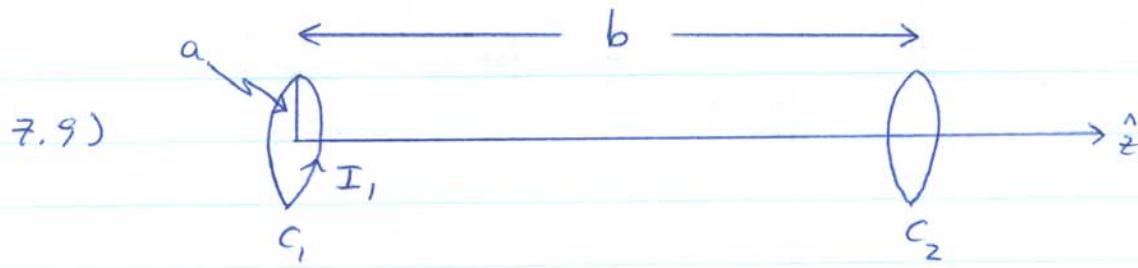
$$= 5.7 \times 10^{-3} \text{ statvolt}$$



Let I_1 be current in C_1 .

Field generated by I_1 at C_2 is

$$\vec{B}_1 \approx \hat{z} \frac{2\pi I_1 a^2}{c(a^2 + b^2)^{3/2}}$$

$$\approx \hat{z} \frac{2\pi I_1 a^2}{c b^3} \quad \text{since } b \gg a.$$


Flux of \vec{B}_1 through C_2 is $\Phi_{21} = \pi a^2 B_1$

Voltage or emf induced in C_2 by current I_1 is

$$\begin{aligned} \mathcal{E}_{21} &= -\frac{1}{c} \frac{d\Phi_{21}}{dt} \\ &= -\frac{1}{c} \pi a^2 \frac{2\pi a^2}{c b^3} \frac{dI_1}{dt} \\ &= -M_{21} \frac{dI_1}{dt} \end{aligned}$$

$$\therefore \text{mutual inductance } M_{21} = \frac{2\pi^2 a^4}{c^2 b^3}.$$

7.13)

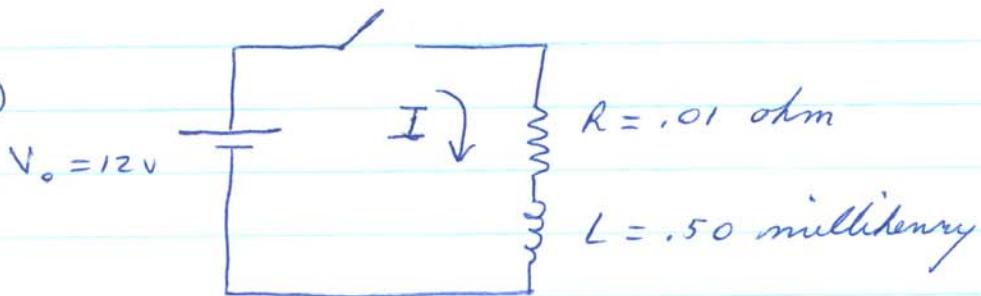

$$V_o = IR + L \frac{dI}{dt}$$

$$L \frac{dI}{dt} = V_o - IR.$$


$$\int_0^I \frac{dI}{V_o - IR} = \int_0^+ \frac{dt}{L}$$

$$-\frac{1}{R} \ln(V_o - IR) \Big|_0^I = \frac{t}{L}$$

$$\ln\left(\frac{V_o - IR}{V_o}\right) = -\frac{Rt}{L}$$

$$1 - \frac{IR}{V_o} = e^{-Rt/L}$$

$$I = \frac{V_o}{R} (1 - e^{-Rt/L}).$$

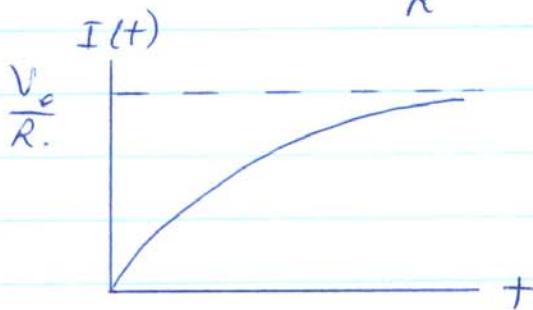

$$I(\infty) = V_o/R.$$

$$, q \frac{V_o}{R} = \frac{V_o}{R} (1 - e^{-Rt/L})$$

$$, q = 1 - e^{-Rt/L}$$

$$e^{-Rt/L} = .1$$

$$\frac{-Rt}{L} = \ln .1$$

$$\therefore t = -\frac{L}{R} \ln .1$$

$$= 2.30 \times \frac{.50 \times 10^{-3} \text{ henry}}{.01 \text{ ohm}}$$

$$= .115 \text{ sec}$$

\therefore current is 90% of its final value after .115 sec.

Energy stored in magnetic field is

$$\frac{1}{2} L I(.115 \text{ sec})^2 = \frac{1}{2} \times .50 \times 10^{-3} \text{ henry} \left(\frac{.9 \times 12 \text{ volts}}{.01 \text{ ohm}} \right)^2 \\ = 292 \text{ joules}$$

Energy supplied by battery up to .115 sec is

$$\int_0^{.115} P dt$$

$$= \int_0^{.115} V_o I(t) dt$$

$$= \int_0^{.115} \frac{V_o^2}{R} (1 - e^{-Rt/L}) dt$$

$$= \frac{V_o^2}{R} \left[t + \frac{L}{R} e^{-Rt/L} \right]_0^{.115}$$

$$= \frac{(12 \text{ v})^2}{.01 \text{ ohm}} \left[.115 + \frac{.50 \times 10^{-3}}{.01} (-.9) \right] = 1008 \text{ joules}$$

7.23) Magnetic field energy density is $\frac{B^2}{8\pi}$.

Total mag. energy in galaxy is

$$\frac{B^2}{8\pi} V_{gal.} = \frac{(3 \times 10^{-6} \text{ gauss})^2}{8\pi} \times \pi \left(\frac{10^{23} \text{ cm}}{2}\right)^2 \times 10^{21} \text{ cm.}$$
$$= 2.8 \times 10^{54} \text{ ergs.}$$

This represents $\frac{2.8 \times 10^{54} \text{ ergs}}{10^{44} \text{ ergs/sec.}}$

$$= 2.8 \times 10^{10} \text{ sec}$$

= 891 yrs. of starlight energy.

7.25) Mag. energy density $\frac{B^2}{8\pi} = \frac{(10^{12} \text{ gauss})^2}{8\pi}$

$$= 4 \times 10^{22} \text{ erg/cm}^3.$$

Energy = mc^2 .

$$\therefore \text{mag. energy density} = \frac{4 \times 10^{22} \text{ erg/cm}^3}{(3 \times 10^{10} \text{ cm/sec})^2}$$
$$= 44.2 \text{ gm/cm}^3.$$