

## Assignment 10 Solutions

1. Current  $I = 10^{10} \frac{\text{elect}}{\text{sec}} \times 1.6 \times 10^{-19} \frac{\text{C}}{\text{elect}} = 1.6 \times 10^{-9} \text{ amp.}$
2. A kettle draws 3 A of DC current when it is connected to a 10 V battery.
  - a) What is the kettle resistance?

$$\begin{aligned} \text{Resistance } R &= \frac{V}{I} \\ &= \frac{10 \text{ V}}{3 \text{ A}} \\ &= 3.33 \text{ ohm.} \end{aligned}$$

- b) What power is supplied to the kettle?

$$\begin{aligned} \text{Power } P &= VI \\ &= 10 \text{ volts} \times 3 \text{ A} \\ &= 30 \text{ watts} \end{aligned}$$

- c) If the kettle has 1 liter of water initially at a temperature of 20 C, how long will it take for the water to be heated to 90C?

$$\begin{aligned} \text{Energy Supplied} &= \text{Energy heat 1l } H_2O \\ \text{in time } t & \quad \text{deg } (90-20)C \\ P t &= 1000 \text{ gm} \times 70C \times 1 \frac{\text{calorie}}{\text{c gm}} \times 4.18 \frac{\text{J}}{\text{cal.}} \\ \uparrow \\ 30 \text{ watts} \end{aligned}$$


$$\begin{aligned} \therefore t &= 9.75 \times 10^3 \text{ sec.} \\ &= 2.7 \text{ hrs.} \end{aligned}$$

This is far from acceptable. One then should go to Tim Horton!

3


A laboratory only has 2 ohm resistors.

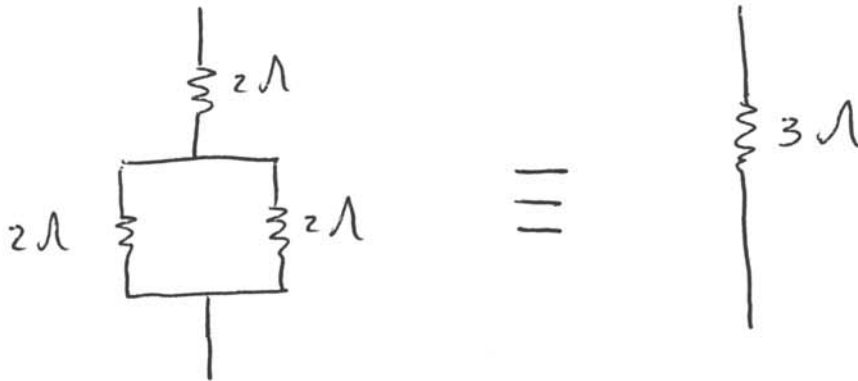a) Draw the circuit required to create a 3 ohm resistance




b) Show that the total power dissipated in the above circuit is the same as when a single 3 ohm resistor is available.

Circuit a

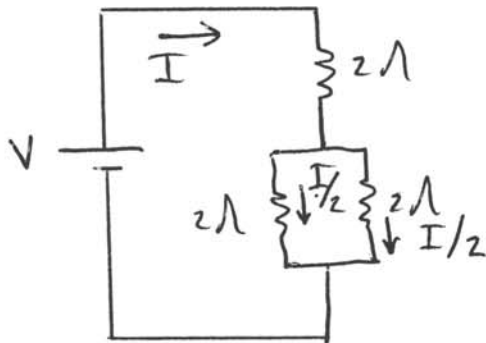

Circuit b

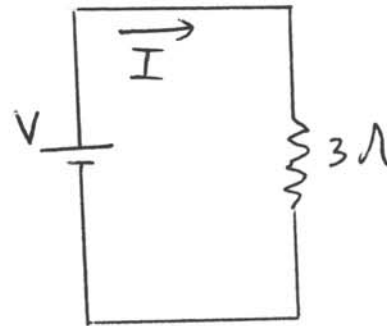In both circuits  $I = \frac{V}{3}$ .

$$\text{Circuit a Power dissipation} = I^2 R + \left(\frac{I}{2}\right)^2 R \times 2$$

$$= \frac{3}{2} I^2 R$$

$$= \frac{3}{2} \left(\frac{V}{3}\right)^2 \times 2$$


$$P_a = \frac{V^2}{3}$$

$$\text{Circuit b Power dissipation} = I^2 \times 3$$

$$P_b = \frac{V^2}{3}$$

$$\therefore P_a = P_b.$$

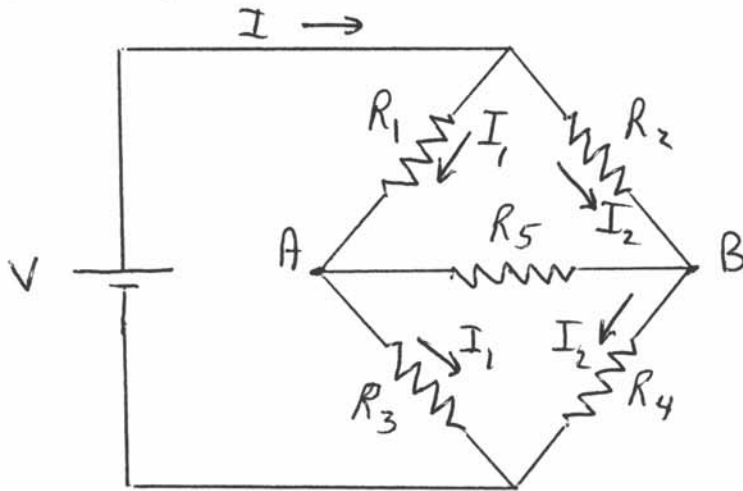- 4 Consider the Wheatstone bridge circuit shown below. Show that no current passes through  $R_5$  if  $R_1 / R_3 = R_2 / R_4$



No current through  $R_5 \Rightarrow V_{AB} = 0$  -

$\therefore$  voltage across  $R_1 =$  voltage across  $R_2$

$$I_1 R_1 = I_2 R_2 \quad (1)$$

also voltage across  $R_3 =$  voltage across  $R_4$

$$I_1 R_3 = I_2 R_4 \quad (2)$$

$$(1) \div (2) \Rightarrow \frac{R_1}{R_3} = \frac{R_2}{R_4}$$