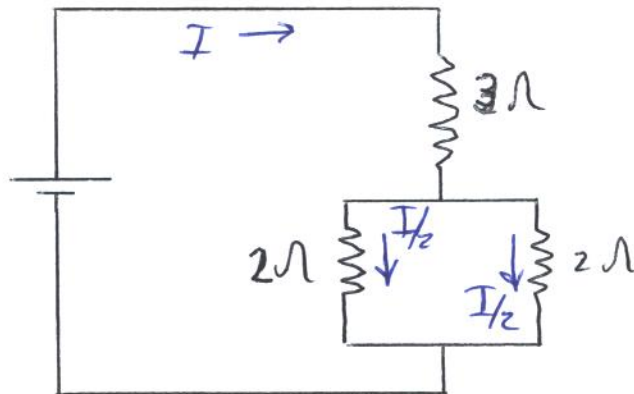


Quiz 10

Name: _____ Student Number: _____

1. A 10 volt battery is connected across two resistors as shown below.



- a) (5 marks) Find the current in each of the resistors.

Two 2Ω resistors in parallel equivalent to $\left(\frac{1}{2} + \frac{1}{2}\right)^{-1} = 1\Omega$ resistor.

$3\Omega + 1\Omega$ resistors in series equivalent to 4Ω .

$$\therefore I = \frac{10 \text{ volt}}{4\Omega} = 2.5 \text{ amp passes through } 3\Omega$$

$$\frac{I}{2} = 1.25 \text{ A passes through each } 2\Omega \text{ resistor.}$$

b) (5 marks) Find the power dissipated in each of the resistors.

Power Dissipated in 3Ω resistor

is $P = I^2 R$

$$= (2.5 \text{ amp})^2 \times 3\Omega$$

$$= 18.75 \text{ watts}$$

Power dissipated in each 2Ω resistor

is $P = (1.25 \text{ amp})^2 \times 2\Omega$

$$= 3.13 \text{ watts}$$

Total = 10 marks